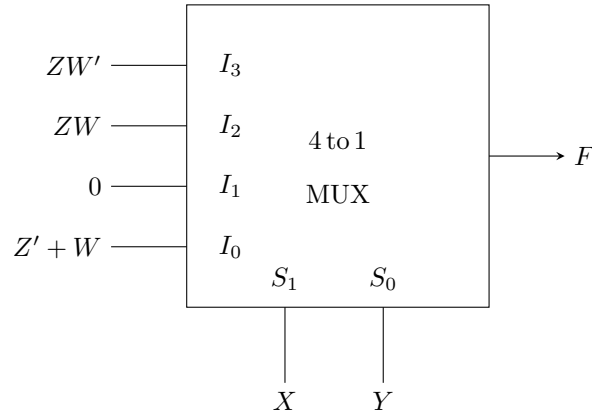


1. A 4×1 multiplexer with two selector lines is used to realize a Boolean function F having four Boolean variables X , Y , Z , and W as shown below. S_0 and S_1 denote the least significant bit (LSB) and most significant bit (MSB) of the selector lines of the multiplexer, respectively. I_0 , I_1 , I_2 , I_3 are the input lines of the multiplexer.



The canonical sum of product representation of F is:

- (A) $F(X, Y, Z, W) = \Sigma m(0, 1, 3, 14, 15)$
- (B) $F(X, Y, Z, W) = \Sigma m(0, 1, 3, 11, 14)$
- (C) $F(X, Y, Z, W) = \Sigma m(2, 5, 9, 11, 14)$
- (D) $F(X, Y, Z, W) = \Sigma m(1, 3, 7, 9, 15)$